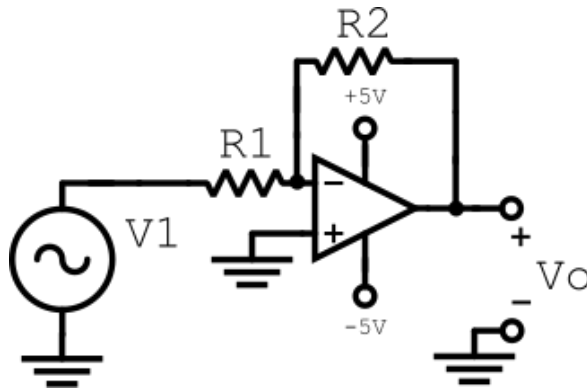


Question 1 (20 minutes - 2 points)

Answer the following questions **with justification**.

- a. Given the following circuit, calculate the peak-to-peak amplitude and the average value of the output voltage V_o .



Data:

Peak-to-peak amplitude of $V_1 = 2 \text{ Vpp}$

Average value of $V_1 = 0 \text{ V}$

Frequency of $V_1 = 1 \text{ kHz}$

$R_1 = 1 \text{ k}\Omega$

$R_2 = 2 \text{ k}\Omega$

Operational Amplifier:

$R_i \rightarrow \infty$

$R_o = 0$

$A_v \rightarrow \infty$

$GBW = 10 \text{ MHz}$

Offset voltage $V_{io} = 100 \text{ mV}$

Offset current $I_{io} = 0 \text{ A}$

Bias current $I_b = 0 \text{ A}$

Peak-to-peak value of V_o :

$$2 \cdot 2 = 4 \text{ Vpp}$$

Average value V_o :

$$0 \cdot 2 + 0.1 \cdot 3 = 0.3 \text{ V}$$

Justification:

$$V_1 = 1 \cdot \sin(2 \cdot \pi \cdot 1000 \cdot t) \text{ V}$$

$$V_o = -\frac{R_2}{R_1} \cdot V_i + (1 + \frac{R_2}{R_1}) \cdot V_{io} = -2 \cdot \sin(2 \cdot \pi \cdot 1000 \cdot t) + 0.3 \text{ V with a maximum of 2.3 V and a minimum of -1.7 V, always between +5 V and -5 V}$$

- b. What does 'Slew Rate' mean in an operational amplifier? Provide an example where the amplifier output is limited by this effect.


It is a rate that defines the maximum slope of the amplifier's output voltage. Typically, it appears when the input voltage is large and changes rapidly. For example, when we try to pass a square wave with an amplitude close to the supply rails through a buffer or voltage follower. At the output, a finite rise and fall slope will be observed, equal to the slew rate, instead of the square wave's vertical edges.

- c. Choose and comment on an advantage of using negative feedback in an electronic amplifier.

One advantage is that it precisely fixes the low-frequency gain of an amplifier. By negatively feeding back, the input voltage or current is compared with another voltage or current proportional to the output, producing an error voltage or current that is amplified. This way, the amplifier remains controlled against internal or external disturbances. The low-frequency gain is determined by the feedback rather than by the amplifier. The precision will depend on how accurate the feedback is.

Other advantages that could be discussed: increases the bandwidth of very slow amplifiers, reduces distortion in non-linear amplifiers, improves input and output impedances.

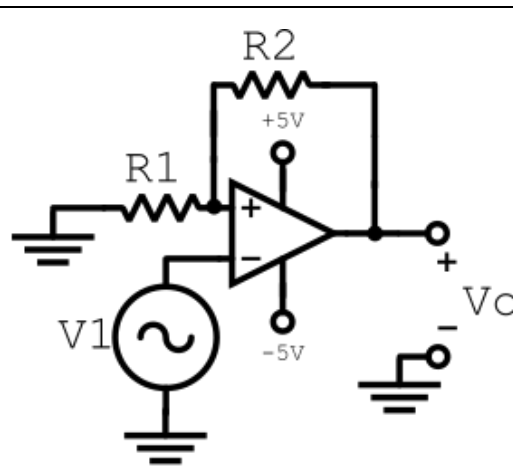- d. Explain the function of this circuit, indicating if it is an amplifier, a comparator, or a filter.



Datos:

Peak-to-peak amplitude of V1 = 2 Vpp

Average value of V1 = 0 V

Frequency of V1 = 1 kHz

R1=1 kΩ

R2=2 kΩ

Operational Amplifier:

$R_i \rightarrow \infty$

$R_o = 0$

$A_v \rightarrow \infty$

GBW=10MHz

Offset voltage $V_{io}=0$ V


Offset voltage $I_{io}=0$ A

Bias current $I_b=0$ A

In this case, it is a comparator. V1 is compared to one-third of Vo, resulting in a comparator with memory or hysteresis loop. The comparison threshold depends on the previous output state, which can be +5V or -5V. The output is always saturated at +5V or -5V because the amplifier gain is infinite.

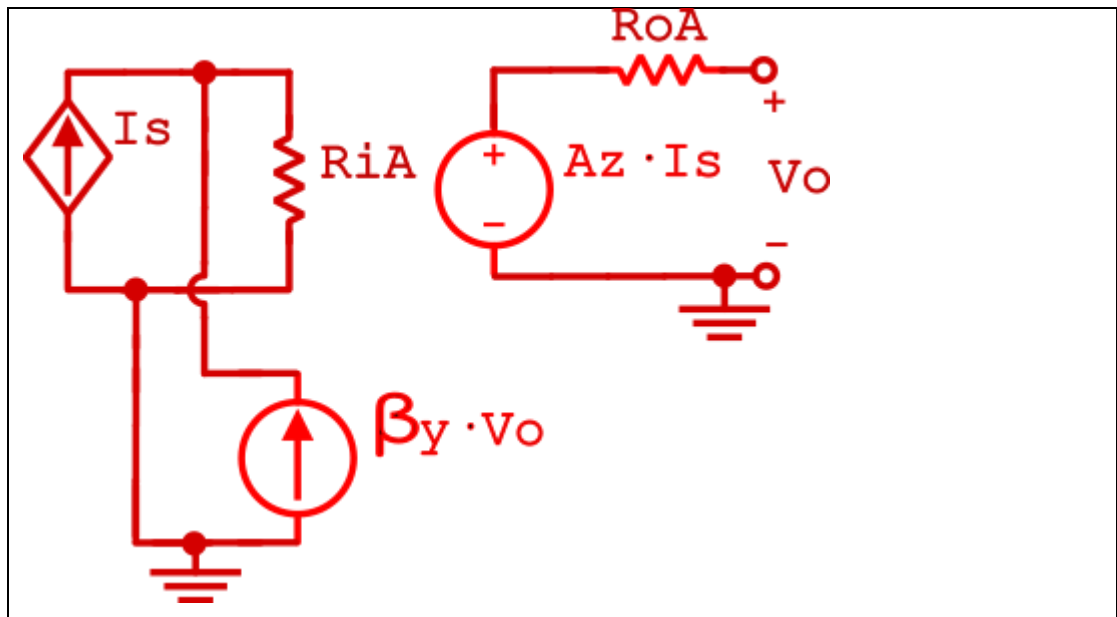
- e. Draw the small-signal model of a transimpedance amplifier with negative feedback, showing the input and output impedances of the non-feedback amplifier, and the

amplification and feedback circuit gains. Assume the feedback circuit does not load the amplifier, or that such loading effects are included in the amplifier's impedances and gain.



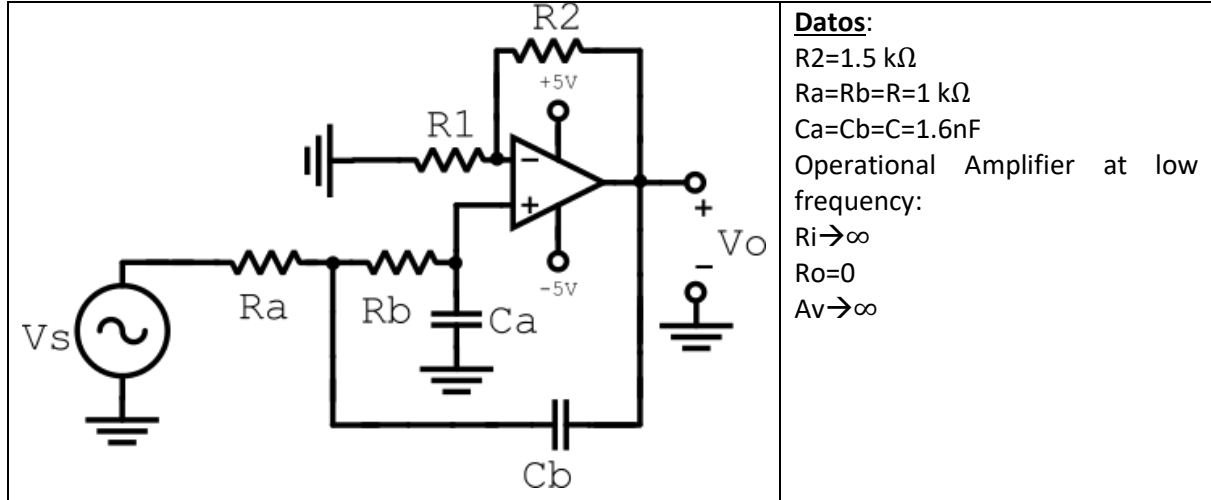Question 2 (40 minutes - 4 points)

Given the low-pass Sallen Key filter in the figure:



El filtro tiene una respuesta en frecuencia dada por:

$$\frac{V_o}{V_s}(j\omega) = \frac{K \cdot (\omega_o)^2}{(j\omega)^2 + \frac{\omega_o}{Q}(j\omega) + \omega_o^2} = \frac{K/(RC)^2}{(j\omega)^2 + \frac{3-K}{RC}(j\omega) + \frac{1}{(RC)^2}}$$

donde K es la ganancia en DC del circuito.

Se pide:

1. Calculate $R1$ to set a DC gain of $5/2$.
2. Calculate the quality factor Q .
3. Calculate the natural frequency of the poles in Hz. Determine whether they are real or complex conjugate poles.
4. Calculate the filter gain at the natural frequency of the poles and express it in dB.
5. Calculate the output voltage if the input voltage has the following expression:

$$V_s = 0.1 \cdot \sin(2 \cdot \pi \cdot 1 \text{ MHz} \cdot t)$$

6. Does the previous result change if the amplifier has an offset voltage of 100mV at the input? If so, calculate it.
7. Which amplifier would you choose to implement this filter: one with a GBW=10kHz or one with a GBW=10MHz? Justify your answer.
8. Could the same frequency response be implemented with a passive filter? Comment on your answer.

②

$$1) K = 1 + \frac{R_2}{R_1} = \frac{5}{2} = 1 + \frac{3}{2} \Rightarrow \frac{R_2}{R_1} = \frac{3}{2} \Rightarrow R_1 = \frac{2}{3} R_2 = 1k\Omega$$

$$2) Q = \frac{1}{3 - \frac{5}{2}} = 2$$

$$3) f_0 = \frac{1}{2\pi RC} = 99.7 \text{ kHz}$$

$$4) \left. \frac{V_o}{V_s} \right|_{\omega=\omega_0} = \left| \frac{k \omega_0^2}{(j\omega_0)^2 + \frac{\omega_0^2}{Q} + \omega_0^2} \right| = k \cdot Q = \frac{5}{2} \cdot 2 = 5$$

$$\approx 14 \text{ dB}$$



5) Cuando $f = 1 \text{ MHz} \Rightarrow$

$$\frac{V_o}{V_s} = \frac{k \cdot (2\pi \cdot 99.7 \text{ kHz})^2}{[j(2\pi \cdot 1 \text{ MHz})]^2 + \frac{2\pi \cdot 99.7 \text{ kHz}}{2} j(2\pi \cdot 1 \text{ MHz}) + (2\pi \cdot 99.7 \text{ kHz})^2}$$

$$= -0.024 - 0.001j \approx 0.024_{180^\circ} \approx -0.024$$

$$V_o = -0.024 \cdot 0.1 \sin(2\pi \cdot 1 \text{ MHz} t) = -2.4 \text{ mV} \sin(2\pi \cdot 1 \text{ MHz} t)$$


6)

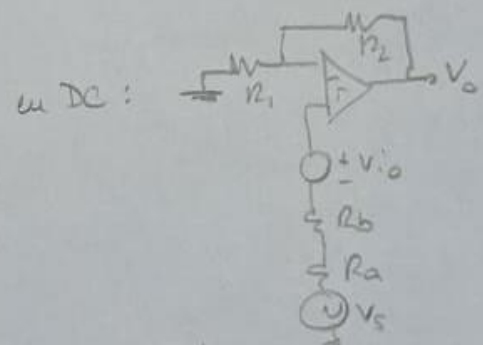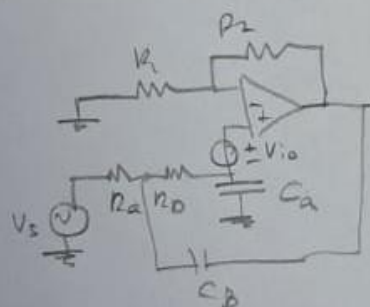

Tenemos que queda en serie y por tanto:
 $V_{io} K = 100 \text{ mV}$, $2.5 = \underline{2.5 \text{ V}}$ a la salida
 $V_o = 2.5 \text{ V} - 2.4 \text{ mV} \sin(2\pi \cdot 1 \text{ MHz} t)$

7) Uno de $GBW = 10\text{MHz}$ ya que el de 10kHz no es suficiente para dar cabida a la respuesta en frecuencia deseada, con lo que pasa a 99.5kHz .

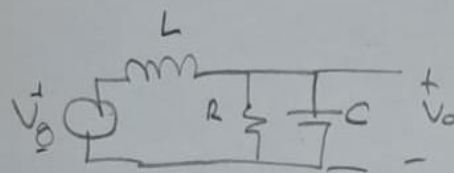
8) Un Aleso pasivo no tiene ganancia de tensión. Se podría implementar con un circuito como:



pero con ganancia $= 1$.

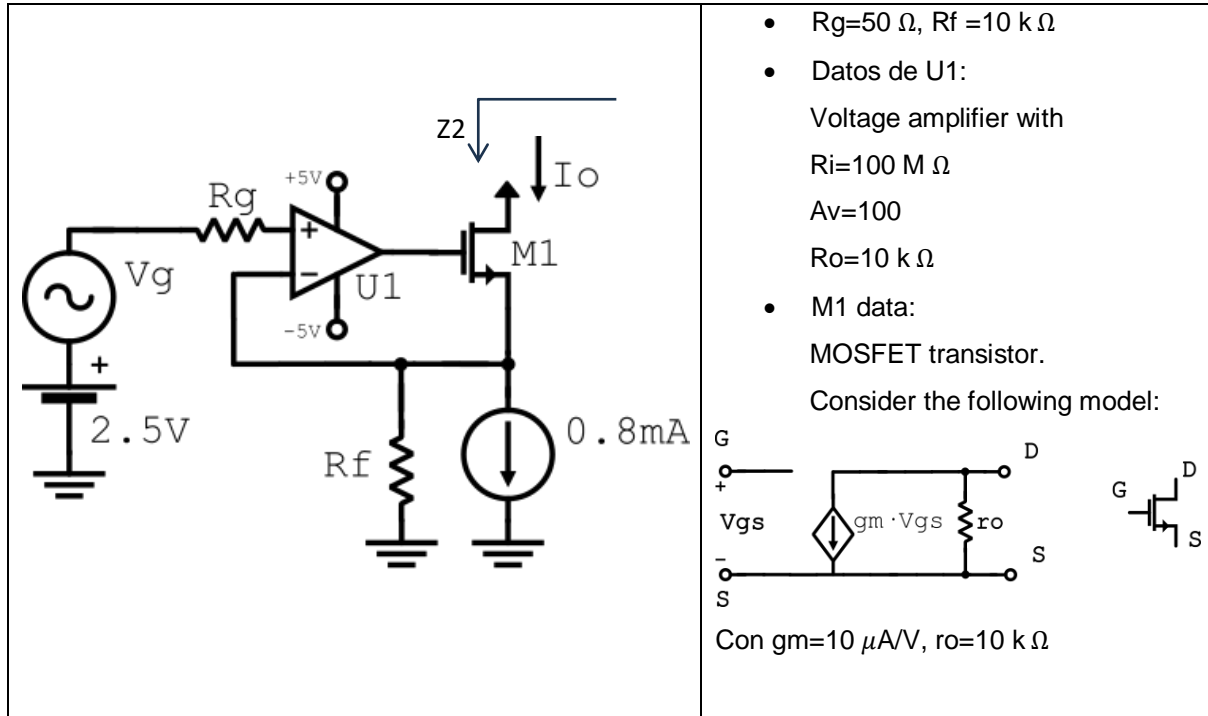Question 3 (40 minutes - 4 points)

The circuit in the figure is a simplified diagram of a voltage-to-current converter. It has a series-series feedback thanks to the R_f resistor.



Tasks:

1. Demonstrate that there is negative feedback in this circuit and identify the amplification and feedback networks.
2. Draw the small-signal model of the circuit. Use the transistor model provided in the figure.
3. Calculate the gain of the β network.
4. Use the previous result to calculate an approximate value for I_o/V_g assuming the loop gain ($A\beta$) is sufficiently large.
5. Draw the small-signal model of the A network, including all loading effects (Network A').
6. Calculate a more realistic value of I_o/V_g and compare it with the result obtained in 4. Consider that in network A', the gain is $500\ \mu\text{A/V}$ and the output impedance is $20\text{ k}\Omega$.
7. Calculate the impedance Z_2 .
8. Indicate whether the output node should be a high or low impedance node and comment on the result obtained in 7.

③

1) Si $I_0 \uparrow \Rightarrow V_{R2} \uparrow \Rightarrow V_- \uparrow \Rightarrow V_i = V_+ - V_- \Rightarrow V_{gsM1} \downarrow \Rightarrow I_{D1} \downarrow$

Series - serie
compensación y
muestra corriente.

(Fuentes de DC ignoradas)


2)

3)

parameter z

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} z_{11} & \beta_2 \\ \beta_1 & z_{22} \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix}$$

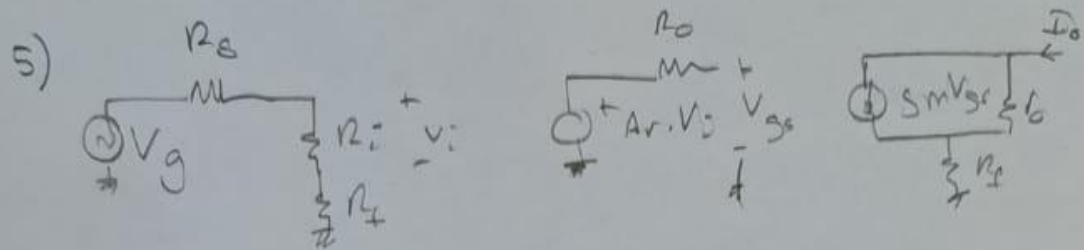4) $\frac{I_0}{V_g} \approx \frac{1}{R_f} = 0.1 \text{ mA/V}$




6)

$$A'_y = \frac{I_o}{V_g} = \frac{I_o}{V_{gs}} \cdot \frac{V_{gs}}{V_i} \cdot \frac{V_i}{V_g}$$

$$\frac{I_o}{V_{gs}} = g_m \frac{r_o}{r_o + R_f}$$

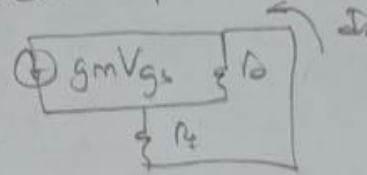(Consideramos el circuito con carga nula. Como la salida es en corriente por tanto un cortocircuito)




$$\frac{V_{gs}}{V_i} = A_v$$

$$\frac{V_i}{V_g} = \frac{R_i}{R_g + R_i + R_f}$$


$$A'_y = g_m \frac{r_o}{r_o + R_f} \cdot A_v \cdot \frac{R_i}{R_g + R_i + R_f} = 10 \mu \frac{10k}{10k + 10k} \cdot 100 \frac{100M}{50 + 100M + 10k}$$
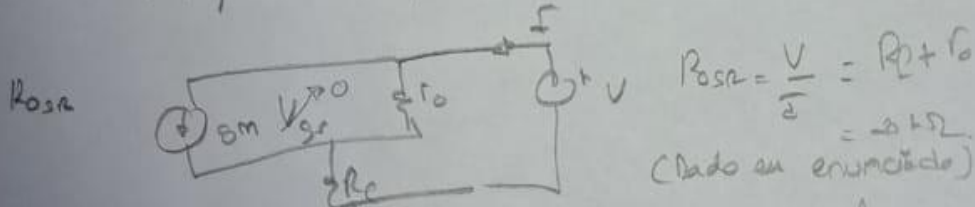
$$= 10 \mu \cdot 500 = 500 \mu A/V \quad (\text{Dado en enunciado})$$



$$R_{out} = \frac{V}{I} = R_f + R_o = 20k\Omega$$

(Dado en enunciado)

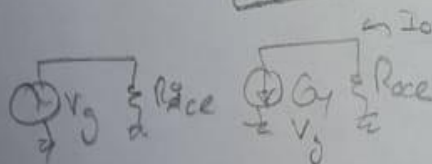


$$\frac{I_o}{V_g} = G_f = \frac{A_y}{1 + A_y R_f} = \frac{500 \mu}{1 + 500 \mu \cdot 10k}$$

$$= \frac{500 \mu}{1 + 5} = 83.3 \mu A/V$$

Idóneamente era 0.1 mA/V

$$7) R_{ocr} = \boxed{R_{ocr} (1 + A\beta) = 20k\Omega \cdot 6 = 120k\Omega}$$

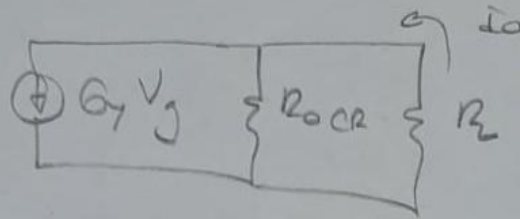8) Debería ser un nodo de alta impedancia ya que la salida es en corriente.



$$I_o = G_y V_g \frac{R_{ocr}}{R_{ocr} + R_L}$$

$$\frac{I_o}{V_g} = G_y \frac{R_{ocr}}{R_{ocr} + R_L} \quad \left. \begin{array}{l} \approx G_y \text{ independiente de } R_L \\ \text{si } R_{ocr} \uparrow \uparrow \end{array} \right\}$$

Por tanto debe ser de alta impedancia